

DN77

Transient and noise protection for Zetex ZXCT series current monitors

by Peter Abiodun Bode, Snr. Applications Engineer

Introduction

Transients are changes in current or voltage which occur in short duration.

Transients can be both internal and external and may not only damage components but also cause a complete system failure if the circuit doesn't have sufficient protection. Transients can either cause catastrophic failures, partial failures or progressive damage to components over a period of time. Internally generated transients may often be energy stored in inductive or capacitive elements which is then released if operating conditions change. Such a transient is created every time an inductive element is switched within a circuit, for example a motor, contactor or relay. Typical internal transient sources are load dumps, inductive switching or ignition pulses.

The interference source is generally referred to as noise when it is not severe enough to cause catastrophic failures but may interfere, or has the potential to interfere, with normal workings of the system.

The Zetex range of current monitors may need to be protected where such transient noise exists. A number of methods are available to do this and these are explored in this document.

Methods of protection

Prevention

Prevention is always better than cure. Hence preventing the transient in the first place, if this is possible, is better than trying to cope with it. Figure 1 shows the ZXCT1008/9 monitoring current through an inductive load. Without the freewheel diode D1, the inductance of the load would have generated a large voltage spike when the transistor switches off. The inclusion of the diode to clamp this voltage and the way it is connected ensures that the current through the coil and current monitor would decay to zero in a controlled manner and the current monitor never sees any noise.

Output series resistance

One method that is particularly suitable for the Zetex 3-terminal devices is again shown in Figure 1. Since these are current output devices, it means that the output transfer function is not adversely affected by the addition of a protective resistance, R_{LIM} , in series with the output pin provided certain circuit parameters are taken into consideration.

For low to moderate transient voltages this resistance, R_{LIM} , is all that is needed for protection.

This needs to be carefully specified as it needs to be high enough to be functional but not too high to compromise normal operation of the device. At the lower end of its value, it is limited by the maximum current that can be supplied by the device. Whilst at the higher end, the limiting factor is the available circuit compliance. The two limits are determined as follows.

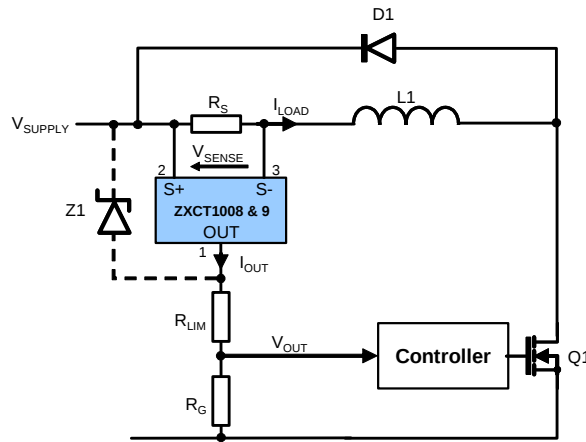


Figure 1 Monitoring current through an inductive load

$$R_{LIM(min)} = \frac{V_{PK} - V_{MAX}}{I_{OUT(max)}} \quad \text{Equation 1}$$

$$R_{LIM(max)} = \frac{R_G (V_{SUPPLY(min)} - (V_{DO} + V_{OUT(max)}))}{V_{OUT(max)}} \quad \text{Equation 2}$$

where,

V_{PK} = Peak transient voltage to be withstood

V_{MAX} = Maximum operating voltage (20V in most cases)

$I_{OUT(max)}$ = Max continuous output current (25mA for ZXCT1008/9)

$V_{SUPPLY(min)}$ = Minimum supply operating voltage,

V_{DO} = Drop-out voltage

$V_{OUT(min)}$ = Maximum required output voltage

For practical determination of R_{LIM} , since the value has to lie between these two limits, pick a value nearest mid-point between them. The mid-point value for R_{LIM} is calculated from,

$$R_{LIM} = \frac{R_{LIM(min)} + R_{LIM(max)}}{2} \quad \text{Equation 3}$$

Adding a zener diode across the current monitor as shown provides better protection by ensuring that the voltage across it is clamped to a known safe value regardless of the amplitude of the transient voltage or R_{LIM} .

RC filtering

If the noise is of a relatively low level, a simple RC filter could be used for protection as shown in Figure 2 and Figure 3 below. This method could be used for any of the current monitors and these two examples specifically demonstrate this for the ZXCT1050 and generically for all others.

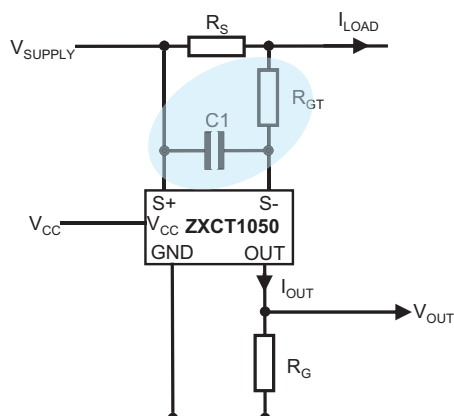


Figure 2 RC noise suppression for ZXCT1050

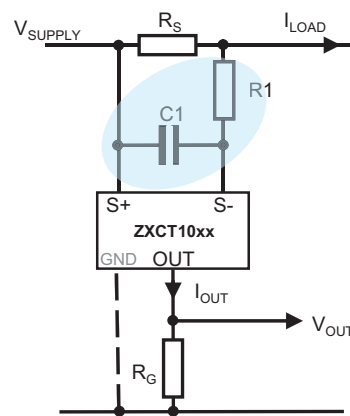


Figure 3 RC noise suppression for a generic current monitor

Notice in Figure 2 that the transconductance resistor is also used as the snubber resistor whilst in most other cases this would be an additional component.

Design example

Consider an application where a 3 Ampere current needs to be measured. 130V transient spikes (Figure 4) are present in the system and a 5V output is required. The supply voltage ranges from 12V to 16V. The device is ZXCT1009 and an output resistance of 10k is required.

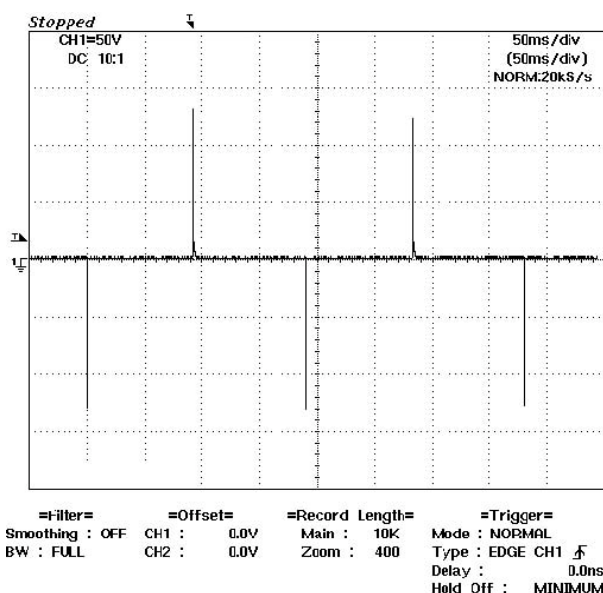


Figure 4 ±130V interference

DN77

Solution:

The solution uses the ZXCT1009 as shown in Figure 5 below.

- First determine R_G as follows

Set V_{SENSE} to 100mV (at 3A this would mean a loss of 300mW in R_S)

Hence,

$$R_S = \frac{V_{SENSE}}{I_{LOAD}} = \frac{0.1}{3} = 33m\Omega$$

Therefore,

$$I_{OUT} = G_T \cdot R_S \cdot I_{LOAD} = 0.001 \cdot 0.033 \cdot 3 = 0.99mA$$

Giving,

$$R_G = \frac{V_{OUT(max)}}{I_{OUT}}$$

- Next determine $R_{LIM(MIN)}$ and $R_{LIM(MAX)}$:

$$R_{LIM(min)} = \frac{V_{PK} - V_{MAX}}{I_{OUT(max)}} = \frac{130V - 20V}{25mA} = 4.4k\Omega$$

$$R_{LIM(max)} = \frac{R_G (V_{SUPPLY(min)} - (V_{DO} + V_{OUT(max)}))}{V_{OUT(max)}} = \frac{5.05(12 - (2.5 + 5))}{5} = 4.545k\Omega$$

As the two values are very close, either value can be used. Hence $R_{LIM} = 4.4k - 4.5k$.

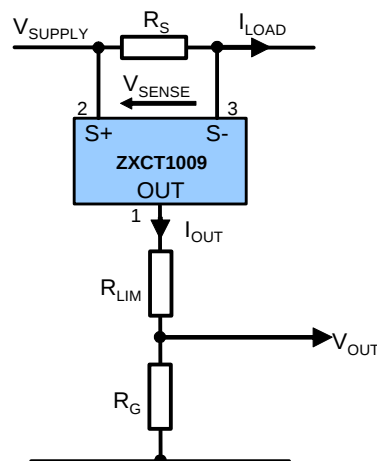


Figure 5 Solution to worked example

Note, that the two values can converge which is also acceptable. If, as can sometimes happen, $R_{LIM(min)}$ is larger than $R_{LIM(max)}$, this would indicate that the maximum output voltage, $V_{OUT(max)}$,

required from the circuit is too high for the set of circumstances. This can be corrected by doing any or all of the following.

- Reduce $V_{OUT(max)}$ this means lowering the value of R_G .
- Increase minimum supply voltage $V_{SUPPLY(min)}$.
- Reduce I_{OUT} (note that, in cases where the transconductance is internally fixed, this can only be done by reducing R_S which will result in an increase in error which may not be desirable).

Conclusion

Protection of current monitors from transients and external noise can be easily achieved with the addition of a few components.

Recommended further reading

1. AN39 - Current Measurement Applications Handbook
2. AN45 - High voltage current monitoring using the ZXCT series in power supplies

DN77

Definitions

Product change

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.zetex.com/salesnetwork

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

Zetex sales offices

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Kustermann-park Balanstraße 59 D-81541 München Germany Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom Telephone: (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

© 2007 Published by Zetex Semiconductors plc