

DN80 Bipolar transistors for MOSFET gate driving applications

Peter Blair, Product Development Manager

Over the last few years MOSFETs have become the device of choice in power switching applications. Whilst on-resistances have significantly reduced, they often require a driver stage to obtain the best performance, particularly when driven from low-voltage, low-current sources. This is where the bipolar transistors inherent advantages excel, as explained below.

Power MOSFETs are often presented as voltage driven devices and as such may be mistakenly expected to be driven from any signal source, irrespective of current capability. This may be an acceptable assumption when driving in DC or very low frequency switching applications where fast edge speeds are not important, but increasingly power MOSFETs are used in switching circuits of hundreds of kHz to 10MHz and in these circumstances the gate charge requirements are a major consideration. The charge necessary to fully enhance a power MOSFET derives from its Gate-Source and Gate-Drain capacitances and is delivered via an external resistor. The Gate voltage follows a characteristic RC time constant which (within EMI constraints) has to be short enough to traverse the linear region without incurring excessive switching losses in the power MOSFET.

The average Gate current during the switching event can be calculated thus:

 $I_G = Q/t$,

where:

 I_G is the average gate current

Q is the total gate charge ($Q_{GS} + Q_{GD}$)

t is the switching transient time (t_{on} or t_{off})

For example a typical 100V, $35m\Omega$ DPAK MOSFET requires approximately 50nC. If it was required to switch in 20ns a Gate current of 2.5 Amps is required.

There are many potential solutions to provide gate drive for power MOSFETs, including dedicated IC drivers, standard logic ICs, discrete MOSFETs and bipolar transistors. The selection criteria for gate driving usually include:

- Switching speed (hence current capability)
- Cost
- Current gain
- Size

Bipolar transistors are eminently suitable for this function as they exhibit fast switching in linear mode, have high pulse current capability, high current density, hence small size and cost.

One of the most popular and cost effective drive circuits is a bipolar, non-inverting totem-pole type driver as shown in Figure 1.

DN80



Figure 1 Totem pole driver stage for power MOSFET

If in the above example the power MOSFET was required to switch at a frequency of 1MHz and driven to $8V_{GS}$ the power dissipation in each driver transistor can be calculated, worst case (assuming Rg = 0), as approximately:

$$\begin{split} \mathsf{P}_{\mathsf{D}(\mathsf{npn})} &= ((\mathsf{V}_{\mathsf{C}\mathsf{C}^-} \, \mathsf{V}_\mathsf{G}/2) \, \bullet \, \mathsf{Q} \, \bullet \, \mathsf{f}) \, + \, (\mathsf{V}_{\mathsf{B}\mathsf{E}} \, \bullet \, \mathsf{I}_\mathsf{B} \, \bullet \, \mathsf{t} \, \bullet \, \mathsf{f}) \\ &= ((12 - 4) \, \bullet \, 50\mathsf{E}^{-9} \, \times \, 1\mathsf{E}^6) \, + \, (0.8 \, \bullet \, 0.8\mathsf{E}^{-3} \, \bullet \, 2\mathsf{E}^{-8} \, \bullet \, 1\mathsf{E}^6) \\ &= 0.4\mathsf{W} \\ \\ \mathsf{P}_{\mathsf{D}(\mathsf{pnp})} &= ((\mathsf{V}_\mathsf{G}/2) \, \bullet \, \mathsf{Q} \, \bullet \, \mathsf{f}) \, + \, (\mathsf{V}_{\mathsf{B}\mathsf{E}} \, \bullet \, \mathsf{I}_\mathsf{B} \, \bullet \, \mathsf{t} \, \bullet \, \mathsf{f}) \\ &= ((4 \, \bullet \, 50\mathsf{E}^{-9} \, \bullet 1\mathsf{E}^6) \, + \, (0.8 \, \bullet \, 0.8\mathsf{E}^{-3} \, \bullet 2\mathsf{E}^{-8} \, \bullet \, 1\mathsf{E}^6) \\ &= 0.2\mathsf{W} \end{split}$$

where:

 P_D is the power dissipation

 V_{CC} is the driver stage supply voltage (assumed in this case to be 12V)

I_G is the average gate current

t is the switching transient time (t_{on} or t_{off})

f is the switching frequency

 $V_{BE(on)}$ is the forward base-emitter voltage

 I_{B} is the transistor base current (I_c/h_{FE})

DN80

With these power losses it is clear that bipolar transistors packaged in small surface mount packages are suitable, preferably co-packaged as complimentary dual devices. Table 1 presents some of the transistors and gate drivers available from Zetex, which are suitable for the gate drive application. Full details of Zetex high speed non-inverting, single MOSFET gate drivers available at <u>www.zetex.com</u>.

Gate drivers							
Device	Package	V _{cc}	I _{SINK(PK)}	ISOURCE	I _{SINK}	Prop. delay	Switching time
		(V)	(A)	(A)	(A)	times	(ns)
				@ I _{IN} = 10mA		(ns)	
ZXGD3001E6	SOT23-6	12	9	4.2	2.2	<3	<11
ZXGD3002E6	SOT23-6	20	9	2.2	2.0	<1.6	<10.8
ZXGD3003E6	SOT23-6	40	5	1.6	1.4	<1.8	<8.9
ZXGD3004E6	SOT23-6	40	8	1.9	1.9	<1.1	<13.4

Single transistors					
Device	Туре	Package	BV _{CEO} (V)	I _{CM} (A)	h _{FE (min)}
ZXTN07012EFF	NPN	SOT23F	12	10	500
ZXTP07012EFF	PNP	SOT23F	12	8	500
ZXTP23015CFH	PNP	SOT23	15	10	250
ZXTN19020DFF	NPN	SOT23F	20	20	300
ZXTP19020CFF	PNP	SOT23F	20	10	250
ZXTN25020DFL	NPN	SOT23	20	8	300
ZXTP25020DFL	PNP	SOT23	20	6	300
ZXTN07045EFF	NPN	SOT23F	45	6	500
ZXTP07040DFF	PNP	SOT23F	40	6	300
ZXTN25040DFL	NPN	SOT23	40	6	300
ZXTP25040DFL	PNP	SOT23	40	5	300
ZXTN2040F	NPN	SOT23	40	2	300
ZXTP2041F	PNP	SOT23	40	2	300
ZXTN19060CFF	NPN	SOT23F	60	12	250
ZXTN2038F	NPN	SOT23	60	2	100

In conclusion, whilst MOSFETs have become the default choice of power switch for many designers bipolar transistors have many useful attributes which can be used beneficially in certain applications. One such application is power MOSFET gate driving, where the bipolar transistor's fast switching in linear mode, high pulse current capability, high current density, and small size and cost make them eminently suitable for this function.

DN80

Definitions

Product change

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

or

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

- 1. are intended to implant into the body
- 2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.
- B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

A

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.zetex.com/salesnetwork

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels. ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:				
"Preview"	Future device intended for production at some point. Samples may be available			
"Active"	Product status recommended for new designs			
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect			
"Not recommended for new designs"	Device is still in production to support existing designs and production			
"Obsolete"	Production has been discontinued			
Datasheet status key:				
"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.			
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.			
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.			
Zetex sales offices				

Europe

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH	Zetex Inc	Zetex (Asia Ltd)	Zetex Semiconductors plc
Kustermann-park	700 Veterans Memorial Highway	3701-04 Metroplaza Tower 1	Zetex Technology Park, Chadderton
Balanstraße 59	Hauppauge, NY 11788	Hing Fong Road, Kwai Fong	Oldham, OL9 9LL
D-81541 München	USA	Hong Kong	United Kingdom
Germany			-
Telefon: (49) 89 45 49 49 0	Telephone: (1) 631 360 2222	Telephone: (852) 26100 611	Telephone: (44) 161 622 4444
Fax: (49) 89 45 49 49 49	Fax: (1) 631 360 8222	Fax: (852) 24250 494	Fax: (44) 161 622 4446
europe.sales@zetex.com	usa.sales@zetex.com	asia.sales@zetex.com	hq@zetex.com

A